

Chapter 5

Capacitance and DC Circuits

5.1 Capacitors

A **capacitor** is a system of *two conductors* that carries *equal and opposite charges*. A capacitor stores charge and energy in the form of electro-static field.

We define **capacitance** as

$$C = \frac{Q}{V} \quad \text{Unit: Farad(F)}$$

where

Q = Charge on one plate


V = Potential difference between the plates

Note: The C of a capacitor is a *constant* that depends only on its shape and material.

i.e. If we increase V for a capacitor, we can increase Q stored.

5.2 Calculating Capacitance

5.2.1 Parallel-Plate Capacitor

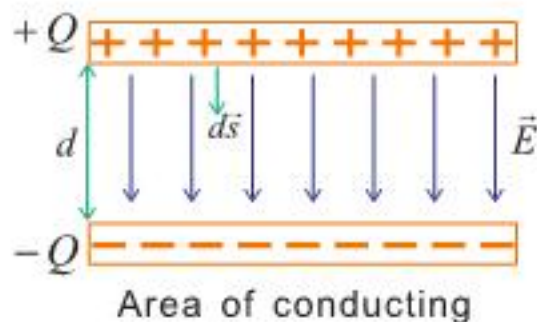

(1) Recall from Chapter 3 note,

$$|\vec{E}| = \frac{\sigma}{\epsilon_0} = \frac{Q}{\epsilon_0 A}$$

(2) Recall from Chapter 4 note,


$$\Delta V = V_+ - V_- = - \int_-^+ \vec{E} \cdot d\vec{s}$$

Again, notice that this integral is independent of the path taken.
 \therefore We can take the path that is parallel to the \vec{E} -field.

$$\begin{aligned} \therefore \Delta V &= \int_+^- \vec{E} \cdot d\vec{s} \\ &= \int_+^- E \cdot ds \\ &= \frac{Q}{\epsilon_0 A} \underbrace{\int_+^- ds}_{\text{Length of path taken}} \\ &= \frac{Q}{\epsilon_0 A} \cdot d \end{aligned}$$

$$(3) \therefore \boxed{C = \frac{Q}{\Delta V} = \frac{\epsilon_0 A}{d}}$$

5.2.2 Cylindrical Capacitor

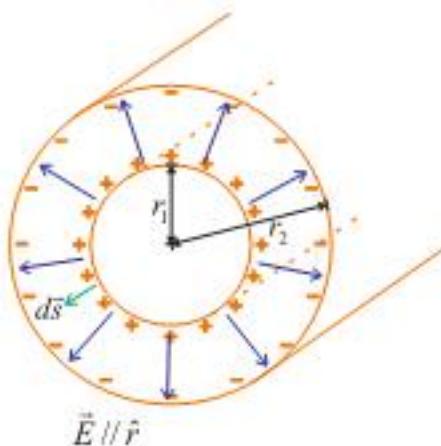

Consider two concentric cylindrical wire of inner and outer radii r_1 and r_2 respectively. The length of the capacitor is L where $r_1 < r_2 \ll L$.

- (1) Using Gauss' Law, we determine that the E-field between the conductors is (cf. Chap3 note)

$$\vec{E} = \frac{1}{2\pi\epsilon_0} \cdot \frac{\lambda}{r} \hat{r} = \frac{1}{2\pi\epsilon_0} \cdot \frac{Q}{Lr} \hat{r}$$

where λ is charge per unit length

- (2)


$$\Delta V = \int_+^- \vec{E} \cdot d\vec{s}$$

Again, we choose the path of integration so that $d\vec{s} \parallel \hat{r} \parallel \vec{E}$

$$\therefore \Delta V = \int_{r_1}^{r_2} E dr = \frac{Q}{2\pi\epsilon_0 L} \underbrace{\int_{r_1}^{r_2} \frac{dr}{r}}_{\ln(\frac{r_2}{r_1})}$$

$$\therefore \boxed{C = \frac{Q}{\Delta V} = 2\pi\epsilon_0 \frac{L}{\ln(r_2/r_1)}}$$

5.2.3 Spherical Capacitor

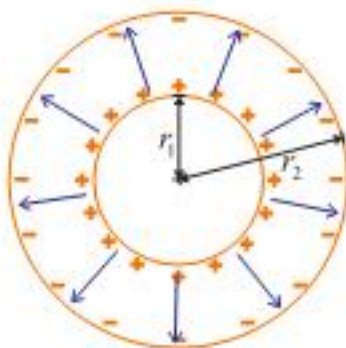

$\vec{E} \parallel \hat{r}$

Choose $d\vec{s} \parallel \hat{r}$

For the space between the two conductors,


$$E = \frac{1}{4\pi\epsilon_0} \cdot \frac{Q}{r^2}; \quad r_1 < r < r_2$$

$$\begin{aligned} \Delta V &= \int_+^- \vec{E} \cdot d\vec{s} \\ \text{Choose } d\vec{s} \parallel \hat{r} &= \int_{r_1}^{r_2} \frac{1}{4\pi\epsilon_0} \cdot \frac{Q}{r^2} dr \\ &= \frac{Q}{4\pi\epsilon_0} \left[\frac{1}{r_1} - \frac{1}{r_2} \right] \end{aligned}$$

$$\boxed{C = 4\pi\epsilon_0 \left[\frac{r_1 r_2}{r_2 - r_1} \right]}$$

5.3 Capacitors in Combination

(a) Capacitors in Parallel

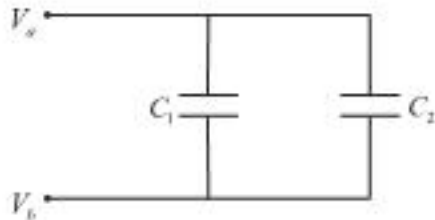


In this case, it's the *potential difference* $V = V_a - V_b$ that is the same across the capacitor.

BUT: Charge on each capacitor different

$$\begin{aligned} \text{Total charge } Q &= Q_1 + Q_2 \\ &= C_1V + C_2V \\ Q &= \underbrace{(C_1 + C_2)}_{\text{Equivalent capacitance}} V \end{aligned}$$

\therefore For capacitors in parallel: $C = C_1 + C_2$

(b) Capacitors in Series

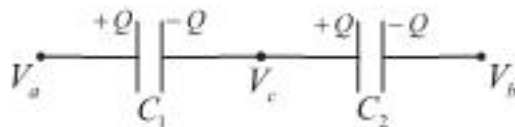

The charge across capacitors are the same.

BUT: Potential difference (P.D.) across capacitors different

$$\begin{aligned} \Delta V_1 &= V_a - V_c = \frac{Q}{C_1} && \text{P.D. across } C_1 \\ \Delta V_2 &= V_c - V_b = \frac{Q}{C_2} && \text{P.D. across } C_2 \end{aligned}$$


\therefore Potential difference

$$\begin{aligned} \Delta V &= V_a - V_b \\ &= \Delta V_1 + \Delta V_2 \\ \Delta V &= Q \left(\frac{1}{C_1} + \frac{1}{C_2} \right) = \frac{Q}{C} \end{aligned}$$

where C is the **Equivalent Capacitance**

$$\therefore \boxed{\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2}}$$

5.4 Energy Storage in Capacitor

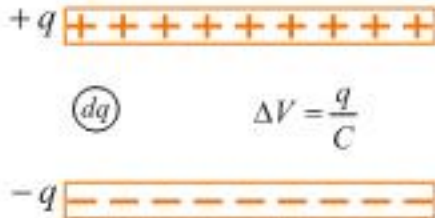

In charging a capacitor, *positive charge* is being moved from the *negative plate* to the *positive plate*.
 \Rightarrow NEEDS WORK DONE!

Suppose we move charge dq from $-ve$ to $+ve$ plate, *change in potential energy*

$$dU = \Delta V \cdot dq = \frac{q}{C} dq$$

Suppose we keep putting in a total charge Q to the capacitor, the *total potential energy*

$$U = \int dU = \int_0^Q \frac{q}{C} dq$$

$$\therefore \boxed{U = \frac{Q^2}{2C} = \frac{1}{2} C \Delta V^2} \quad (\because Q=C\Delta V)$$

The energy stored in the capacitor is stored in the **electric field** between the plates.

Note : In a parallel-plate capacitor, the *E-field is constant between the plates*.

\therefore We can consider the E-field energy

$$\text{density } u = \frac{\text{Total energy stored}}{\text{Total volume with E-field}}$$

$$\therefore u = \frac{U}{\underbrace{Ad}_{\text{Rectangular volume}}}$$

Recall

$$\begin{cases} C = \frac{\epsilon_0 A}{d} \\ E = \frac{\Delta V}{d} \Rightarrow \Delta V = Ed \end{cases}$$


$$\therefore u = \frac{1}{2} \left(\frac{\epsilon_0 A}{d} \right) \cdot (Ed)^2 \cdot \frac{1}{Ad}$$

$$\boxed{u = \frac{1}{2} \epsilon_0 E^2}$$

↑
can be generally applied

Energy per unit volume
of the electrostatic field

Example : Changing capacitance

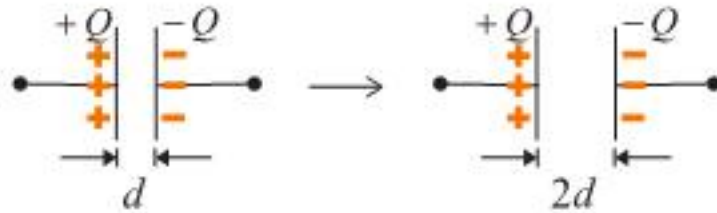

(1) Isolated Capacitor:

Charge on the capacitor plates remains *constant*.

BUT: $C_{new} = \frac{\epsilon_0 A}{2d} = \frac{1}{2} C_{old}$

$$\therefore U_{new} = \frac{Q^2}{2C_{new}} = \frac{Q^2}{2C_{old}/2} = 2U_{old}$$

\therefore In pulling the plates apart, work done $W > 0$

Summary :

$$\begin{array}{l} (V = \frac{Q}{C}) \Rightarrow \\ \frac{1}{2} \epsilon_0 E^2 = \end{array} \begin{array}{l} Q \rightarrow Q \\ V \rightarrow 2V \\ u \rightarrow u \end{array} \quad \begin{array}{l} C \rightarrow C/2 \\ E \rightarrow E \\ U \rightarrow 2U \end{array} \quad \begin{array}{l} (E = \frac{V}{d}) \\ (U = u \cdot \text{volume}) \end{array}$$

(2) Capacitor connected to a battery:


Potential difference between capacitor plates remains *constant*.

$$U_{new} = \frac{1}{2} C_{new} \Delta V^2 = \frac{1}{2} \cdot \frac{1}{2} C_{old} \Delta V^2 = \frac{1}{2} U_{old}$$

\therefore In pulling the plates apart, work done by battery < 0


Summary :
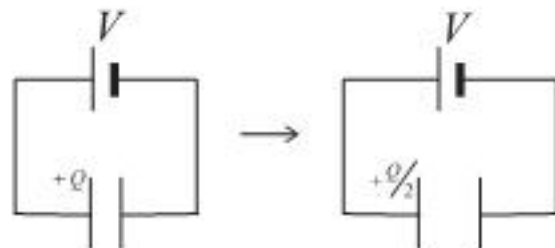
$$\begin{array}{l} Q \rightarrow Q/2 \\ V \rightarrow V \\ u \rightarrow u/4 \end{array} \quad \begin{array}{l} C \rightarrow C/2 \\ E \rightarrow E/2 \\ U \rightarrow U/2 \end{array}$$



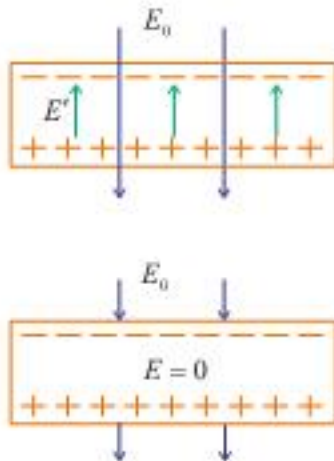5.5 Dielectric Constant

We first recall the case for a *conductor* being placed in an *external E-field* E_0 .



In a conductor, charges are free to move inside so that the *internal E-field* E' set up by these charges





$$E' = -E_0$$

so that E-field inside conductor = 0.

Generally, for **dielectric**, the atoms and molecules behave like a **dipole** in an E-field.



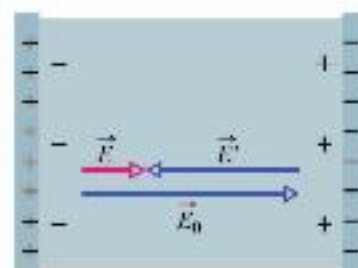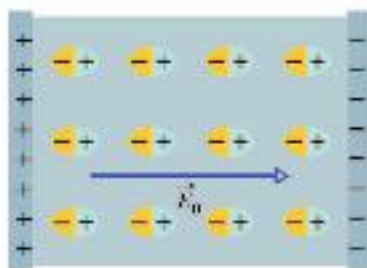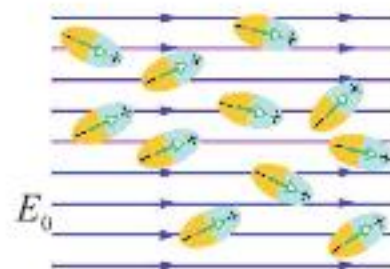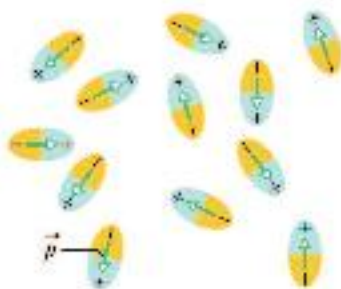Or, we can envision this so that in the absence of E-field, the *direction of dipole in the dielectric* are randomly distributed.



The aligned dipoles will generate an *induced E-field* E' , where $|E'| < |E_0|$. We can observe the aligned dipoles in the form of *induced surface charge*.

Dielectric Constant : When a dielectric is placed in an external E-field E_0 , the E-field inside a dielectric is *induced*.
E-field in dielectric

$$E = \frac{1}{K_e} E_0$$

$$K_e = \text{dielectric constant} \geq 1$$

Example :

Vacuum	$K_e = 1$
Porcelain	$K_e = 6.5$
Water	$K_e \sim 80$
Perfect conductor	$K_e = \infty$
Air	$K_e = 1.00059$

5.6 Capacitor with Dielectric

Case I :



Again, the *charge remains constant* after dielectric is inserted.

BUT: $E_{new} = \frac{1}{K_e} E_{old}$

$$\therefore \Delta V = Ed \Rightarrow \Delta V_{new} = \frac{1}{K_e} \Delta V_{old}$$

$$\therefore C = \frac{Q}{\Delta V} \Rightarrow C_{new} = K_e C_{old}$$

For a parallel-plate capacitor with dielectric:

$$C = \frac{K_e \epsilon_0 A}{d}$$

We can also write $C = \frac{\epsilon A}{d}$ in general with

$$\epsilon = K_e \epsilon_0 \quad (\text{called permittivity of dielectric})$$


(Recall $\epsilon_0 = \text{Permittivity of free space}$)

$$\text{Energy stored } U = \frac{Q^2}{2C};$$

$$\therefore U_{\text{new}} = \frac{1}{K_e} U_{\text{old}} < U_{\text{old}}$$

$$\therefore \text{Work done in inserting dielectric} < 0$$

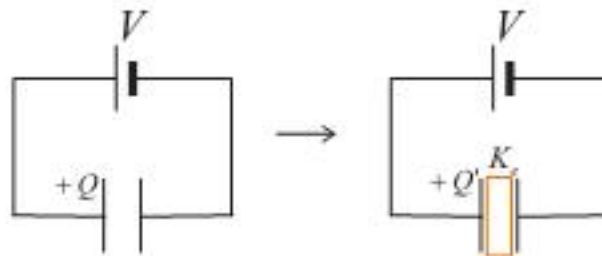Case II : Capacitor connected to a battery



Voltage across capacitor plates *remains constant* after insertion of dielectric.

In both scenarios, the E-field inside capacitor remains constant
 $(\because E = V/d)$

BUT: How can E-field remain constant?

ANSWER: By having extra charge on capacitor plates.

Recall: For conductors,

$$E = \frac{\sigma}{\epsilon_0} \quad (\text{Chapter 3 note})$$

$$\Rightarrow E = \frac{Q}{\epsilon_0 A} \quad (\sigma = \text{charge per unit area} = Q/A)$$

After insertion of dielectric:

$$E' = \frac{E}{K_e} = \frac{Q'}{K_e \epsilon_0 A}$$

But E-field remains constant!

$$\therefore E' = E \Rightarrow \frac{Q'}{K_e \epsilon_0 A} = \frac{Q}{\epsilon_0 A}$$


$$\Rightarrow Q' = K_e Q > Q$$

$$\begin{aligned} \therefore \text{Capacitor } C = Q/V &\Rightarrow C' \rightarrow K_e C \\ \text{Energy stored } U = \frac{1}{2} CV^2 &\Rightarrow U' \rightarrow K_e U \\ (\text{i.e. } U_{\text{new}} > U_{\text{old}}) & \end{aligned}$$

$$\therefore \text{Work done to insert dielectric} > 0$$

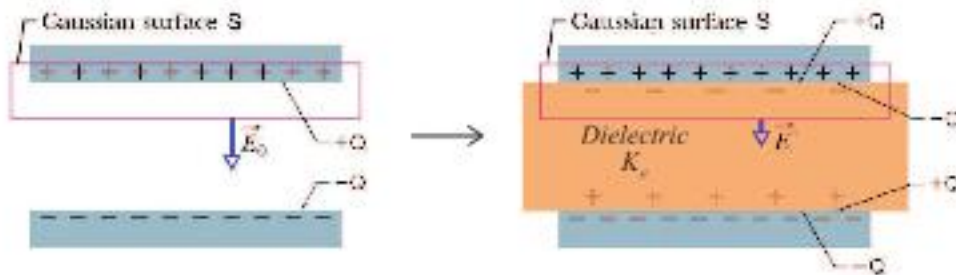5.7 Gauss' Law in Dielectric

The Gauss' Law we've learned is applicable in *vacuum only*. Let's use the capacitor as an example to examine Gauss' Law in dielectric.



Free charge on plates	$\pm Q$	$\pm Q$
Induced charge on dielectric	0	$\mp Q'$

$$\begin{aligned} \text{Gauss' Law} \quad \oint_S \vec{E} \cdot d\vec{A} &= \frac{Q}{\epsilon_0} & \text{Gauss' Law:} \quad \oint_S \vec{E}' \cdot d\vec{A} &= \frac{Q - Q'}{\epsilon_0} \\ \Rightarrow E_0 &= \frac{Q}{\epsilon_0 A} \quad (1) & \therefore E' &= \frac{Q - Q'}{\epsilon_0 A} \quad (2) \end{aligned}$$

However, we define $E' = \frac{E_0}{K_e}$ (3)

From (1), (2), (3) $\therefore \frac{Q}{K_e \epsilon_0 A} = \frac{Q}{\epsilon_0 A} - \frac{Q'}{\epsilon_0 A}$

$$\therefore \text{Induced charge density } \sigma' = \frac{Q'}{A} = \sigma \left(1 - \frac{1}{K_e}\right) < \sigma$$

where σ is free charge density.

Recall Gauss' Law in Dielectric:

$$\begin{array}{ccccc} \epsilon_0 \oint_S \vec{E}' \cdot d\vec{A} & = & Q & - & Q' \\ \uparrow & & \uparrow & & \uparrow \\ \text{E-field in dielectric} & & \text{free charge} & & \text{induced charge} \end{array}$$

$$\Rightarrow \epsilon_0 \oint_S \vec{E}' \cdot d\vec{A} = Q - Q\left[1 - \frac{1}{K_e}\right]$$

$$\Rightarrow \epsilon_0 \oint_S \vec{E}' \cdot d\vec{A} = \frac{Q}{K_e}$$

$$\boxed{\oint_S K_e \vec{E}' \cdot d\vec{A} = \frac{Q}{\epsilon_0}} \quad \text{Gauss' Law in dielectric}$$

Note :

- (1) This goes back to the Gauss' Law in vacuum with $E = \frac{E_0}{K_e}$ for dielectric
- (2) Only *free charges* need to be considered, even for dielectric where there are *induced charges*.
- (3) Another way to write:

$$\oint_S \vec{E} \cdot d\vec{A} = \frac{Q}{\epsilon}$$

where \vec{E} is E-field in dielectric, $\epsilon = K_e \epsilon_0$ is Permittivity

Energy stored with dielectric:

$$\text{Total energy stored: } U = \frac{1}{2} CV^2$$

$$\text{With dielectric, recall } C = \frac{K_e \epsilon_0 A}{d}$$

$$V = Ed$$

\therefore Energy stored per unit volume:

$$\boxed{u_e = \frac{U}{Ad} = \frac{1}{2} K_e \epsilon_0 E^2}$$

$$\text{and } u_{\text{dielectric}} = K_e u_{\text{vacuum}}$$

\therefore More energy is stored per unit volume in dielectric than in vacuum.

5.8 Ohm's Law and Resistance

ELECTRIC CURRENT is defined as the flow of electric charge through a cross-sectional area.

$$\boxed{i = \frac{dQ}{dt}} \quad \begin{array}{l} \text{Unit: Ampere (A)} \\ = \text{C/second} \end{array}$$

Convention :


- (1) Direction of current is the direction of *flow of positive charge*.
- (2) Current is NOT a vector, but the **current density** is a **vector**.

\vec{j} = charge flow per unit time per unit area

$$\boxed{i = \int \vec{j} \cdot d\vec{A}}$$

Drift Velocity :

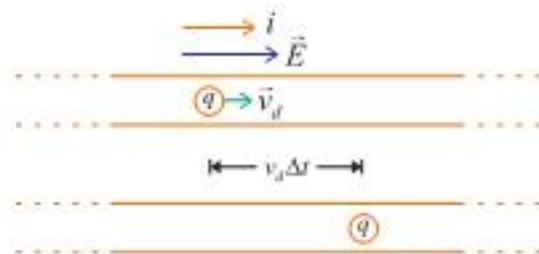Consider a current i flowing through a cross-sectional area A :



\therefore In time Δt , total charges passing through segment:

$$\Delta Q = q \underbrace{A(v_d \Delta t)}_{\text{Volume of charge passing through}} n$$

where q is charge of the current carrier, n is density of charge carrier per unit volume

$$\therefore \text{Current: } \boxed{i = \frac{\Delta Q}{\Delta t} = nqAv_d}$$

$$\text{Current Density: } \boxed{\vec{j} = nq\vec{v}_d}$$

Note : For metal, the charge carriers are the free electrons inside.

$\therefore \vec{j} = -ne\vec{v}_d$ for metals

\therefore Inside metals, \vec{j} and \vec{v}_d are in *opposite direction*.

We define a general property, **conductivity** (σ), of a material as:

$$\boxed{\vec{j} = \sigma \vec{E}}$$

Note : In general, σ is NOT a constant number, but rather a *function of position and applied E-field*.

A more commonly used property, **resistivity** (ρ), is defined as $\rho = \frac{1}{\sigma}$

$$\therefore \vec{E} = \rho \vec{j}$$


Unit of ρ : Ohm-meter (Ωm)
where Ohm (Ω) = Volt/Ampere

OHM'S LAW:

Ohmic materials have resistivity that are *independent of the applied electric field*.
i.e. metals (in not too high E-field)

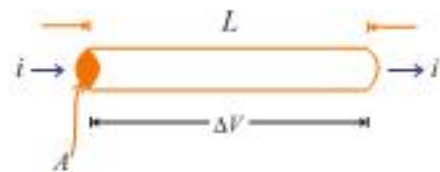Example :

Consider a **resistor** (ohmic material) of length L and cross-sectional area A .



\therefore Electric field inside conductor:

$$\Delta V = \int \vec{E} \cdot d\vec{s} = E \cdot L \Rightarrow E = \frac{\Delta V}{L}$$


Current density: $j = \frac{i}{A}$

$$\begin{aligned} \therefore \rho &= \frac{E}{j} \\ \rho &= \frac{\Delta V}{L} \cdot \frac{1}{i/A} \end{aligned}$$

$$\boxed{\frac{\Delta V}{i} = R = \rho \frac{L}{A}}$$

where R is the **resistance** of the conductor.

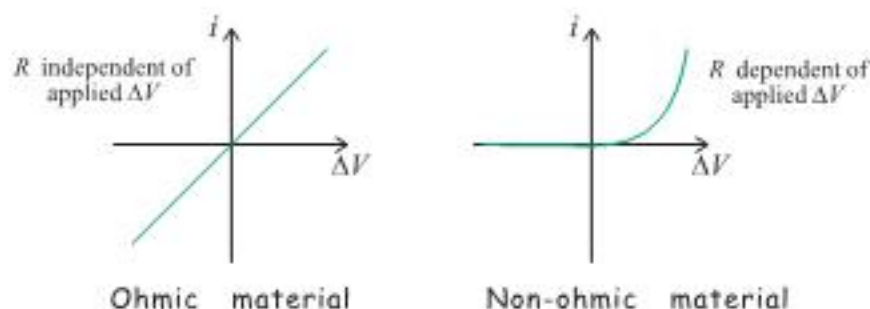
Note: $\Delta V = iR$ is NOT a statement of Ohm's Law. It's just a definition for resistance.



(Read Chap. 29-4 of Halliday Vol 2)

ENERGY IN CURRENT:

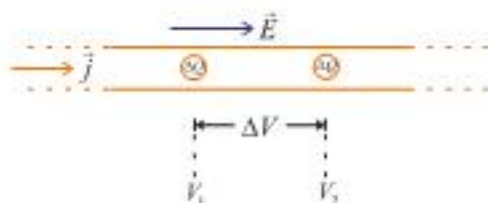Assuming a charge ΔQ enters with potential V_1 and leaves with potential V_2 :



∴ Potential energy lost in the wire:

$$\begin{aligned}\Delta U &= \Delta Q V_2 - \Delta Q V_1 \\ \Delta U &= \Delta Q(V_2 - V_1)\end{aligned}$$

∴ Rate of energy lost per unit time

$$\frac{\Delta U}{\Delta t} = \frac{\Delta Q}{\Delta t} (V_2 - V_1)$$

Joule's heating


$$P = i \cdot \Delta V = \text{Power dissipated in conductor}$$

For a resistor R , $P = i^2 R = \frac{\Delta V^2}{R}$

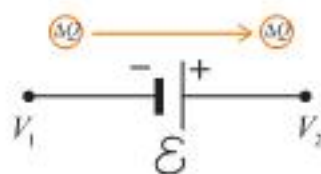5.9 DC Circuits


A **battery** is a device that *supplies electrical energy* to maintain a current in a circuit.

In moving from point 1 to 2, electric potential energy increase by $\Delta U = \Delta Q(V_2 - V_1) = \text{Work done by } \mathcal{E}$



Define $\mathcal{E} = \text{Work done/charge} = V_2 - V_1$

Example :

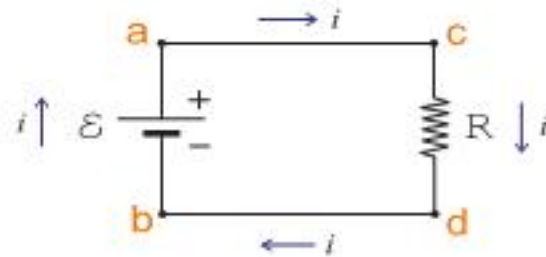


$$\left. \begin{array}{l} V_a = V_c \\ V_b = V_d \end{array} \right\} \text{ assuming}^{(1)} \text{ perfect conducting wires.}$$

$$\begin{aligned} \text{By Definition: } V_c - V_d &= iR \\ V_a - V_b &= \mathcal{E} \end{aligned}$$

$$\therefore \mathcal{E} = iR \Rightarrow i = \frac{\mathcal{E}}{R}$$

Also, we have assumed⁽²⁾ zero resistance inside battery.

Resistance in combination :

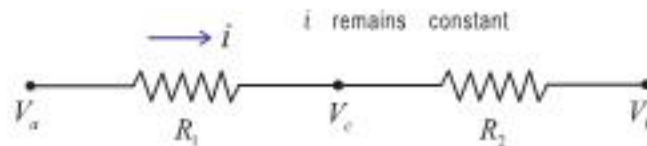


Potential difference (P.D.)


$$\begin{aligned} V_a - V_b &= (V_a - V_c) + (V_c - V_b) \\ &= iR_1 + iR_2 \end{aligned}$$

\therefore Equivalent Resistance
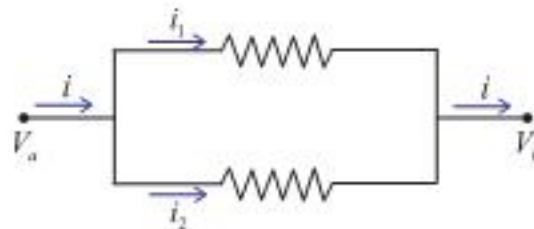
$$\begin{aligned} R &= R_1 + R_2 && \text{for resistors in series} \\ \frac{1}{R} &= \frac{1}{R_1} + \frac{1}{R_2} && \text{for resistors in parallel} \end{aligned}$$



Example :

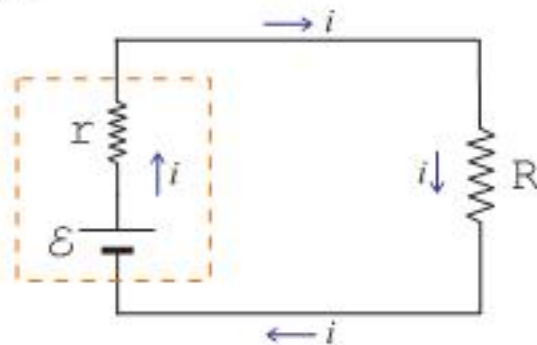

For real battery, there is an **internal resistance** that we cannot ignore.

$$\begin{aligned}\therefore \mathcal{E} &= i(R+r) \\ i &= \frac{\mathcal{E}}{R+r}\end{aligned}$$

Joule's heating in resistor R :


$$\begin{aligned}P &= i \cdot (\text{P.D. across resistor } R) \\ &= i^2 R \\ P &= \frac{\mathcal{E}^2 R}{(R+r)^2}\end{aligned}$$

Question: What is the value of R to obtain *maximum* Joule's heating?

Answer: We want to find R to *maximize* P .

$$\frac{dP}{dR} = \frac{\mathcal{E}^2}{(R+r)^2} - \frac{\mathcal{E}^2 2R}{(R+r)^3}$$
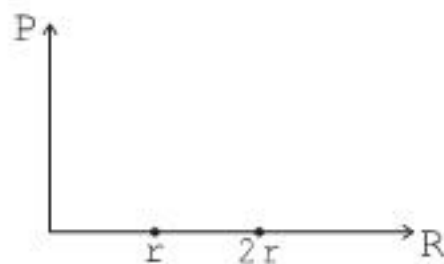
$$\begin{aligned}\text{Setting } \frac{dP}{dR} = 0 &\Rightarrow \frac{\mathcal{E}^2}{(R+r)^3} [(R+r) - 2R] = 0 \\ &\Rightarrow r - R = 0 \\ &\Rightarrow R = r\end{aligned}$$



ANALYSIS OF COMPLEX CIRCUITS:

KIRCHOFF'S LAWS:

- (1) First Law (Junction Rule):

Total current entering a junction equal to the total current leaving the junction.




- (2) Second Law (Loop Rule):

The sum of potential differences around a complete circuit loop is zero.

Convention :


(i)

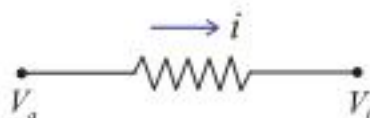

$$V_a > V_b \Rightarrow \text{Potential difference} = -iR$$

i.e. Potential *drops* across resistors


(ii)

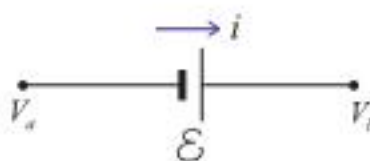

$$V_b > V_a \Rightarrow \text{Potential difference} = +\mathcal{E}$$

i.e. Potential *rises* across the negative plate of the battery.

Example :

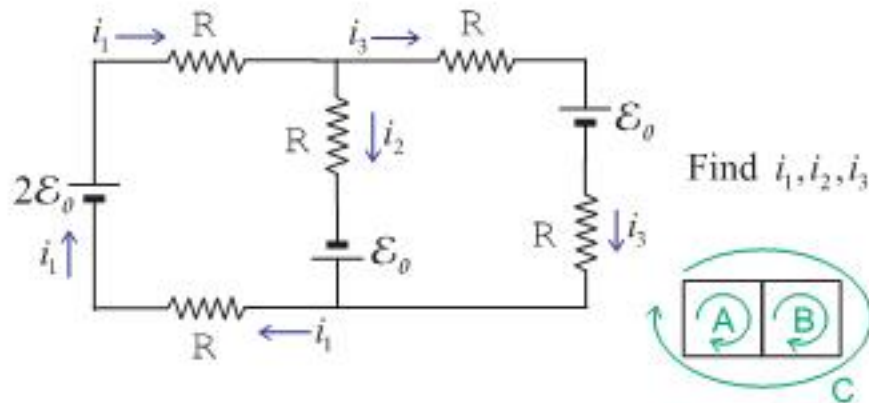

By junction rule:

$$i_1 = i_2 + i_3 \quad (5.1)$$

By loop rule:

$$\text{Loop A} \Rightarrow 2\mathcal{E}_0 - i_1 R - i_2 R + \mathcal{E}_0 - i_1 R = 0 \quad (5.2)$$

$$\text{Loop B} \Rightarrow -i_3 R - \mathcal{E}_0 - i_3 R - \mathcal{E}_0 + i_2 R = 0 \quad (5.3)$$

$$\text{Loop C} \Rightarrow 2\mathcal{E}_0 - i_1 R - i_3 R - \mathcal{E}_0 - i_3 R - i_1 R = 0 \quad (5.4)$$

BUT: $(5.4) = (5.2) + (5.3)$

General rule: Need only 3 equations for 3 current

$$i_1 = i_2 + i_3 \quad (5.1)$$

$$3\mathcal{E}_0 - 2i_1 R - i_2 R = 0 \quad (5.2)$$

$$-2\mathcal{E}_0 + i_2 R - 2i_3 R = 0 \quad (5.3)$$

Substitute (5.1) into (5.2) :

$$\begin{aligned} 3\mathcal{E}_0 - 2(i_2 + i_3)R - i_2 R &= 0 \\ \Rightarrow 3\mathcal{E}_0 - 3i_2 R - 2i_3 R &= 0 \end{aligned} \quad (5.4)$$

Subtract (5.3) from (5.4), i.e. $(5.4) - (5.3)$

$$3\mathcal{E}_0 - (-2\mathcal{E}_0) - 3i_2 R - i_2 R = 0$$

$$\Rightarrow \boxed{i_2 = \frac{5}{4} \cdot \frac{\mathcal{E}_0}{R}}$$

Substitute i_2 into (5.3) :

$$-2\mathcal{E}_0 + \left(\frac{5}{4} \cdot \frac{\mathcal{E}_0}{R}\right)R - 2i_3 R = 0$$

$$\Rightarrow \boxed{i_3 = -\frac{3}{8} \cdot \frac{\mathcal{E}_0}{R}}$$


Substitute i_2, i_3 into (5.1) :

$$\boxed{i_1 = \left(\frac{5}{4} - \frac{3}{8}\right) \frac{\mathcal{E}_0}{R} = \frac{7}{8} \cdot \frac{\mathcal{E}_0}{R}}$$

Note: A *negative* current means that it is flowing in *opposite direction* from the one assumed.

5.10 RC Circuits

(A) *Charging* a capacitor with battery:

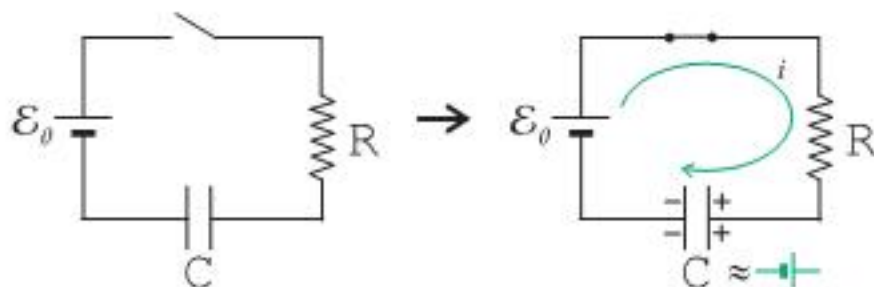

Using the loop rule:

$$+\mathcal{E}_0 - \underbrace{iR}_{\substack{\text{P.D.} \\ \text{across } R}} - \underbrace{\frac{Q}{C}}_{\substack{\text{P.D.} \\ \text{across } C}} = 0$$

Note: Direction of i is chosen so that the current represents the rate at which the charge on the capacitor is *increasing*.

$$\begin{aligned} \therefore \mathcal{E} &= R \frac{dQ}{dt} + \frac{Q}{C} && \text{1st order} \\ &&& \text{differential eqn.} \\ \Rightarrow \frac{dQ}{\mathcal{E}C - Q} &= \frac{dt}{RC} \end{aligned}$$

Integrate both sides and use the initial condition:

$t = 0, \quad Q \text{ on capacitor} = 0$

$$\int_0^Q \frac{dQ}{\mathcal{E}C - Q} = \int_0^t \frac{dt}{RC}$$


$$\begin{aligned}
 -\ln(\mathcal{E}C - Q)\Big|_0^Q &= \frac{t}{RC}\Big|_0^t \\
 \Rightarrow -\ln(\mathcal{E}C - Q) + \ln(\mathcal{E}C) &= \frac{t}{RC} \\
 \Rightarrow \ln\left(\frac{1}{1 - \frac{Q}{\mathcal{E}C}}\right) &= \frac{t}{RC} \\
 \Rightarrow \frac{1}{1 - \frac{Q}{\mathcal{E}C}} &= e^{t/RC} \\
 \Rightarrow \frac{Q}{\mathcal{E}C} &= 1 - e^{-t/RC} \\
 \Rightarrow \boxed{Q(t) = \mathcal{E}C(1 - e^{-t/RC})}
 \end{aligned}$$

Note: (1) At $t = 0$, $Q(t = 0) = \mathcal{E}C(1 - 1) = 0$

(2) As $t \rightarrow \infty$, $Q(t \rightarrow \infty) = \mathcal{E}C(1 - 0) = \mathcal{E}C$
 = Final charge on capacitor (Q_0)

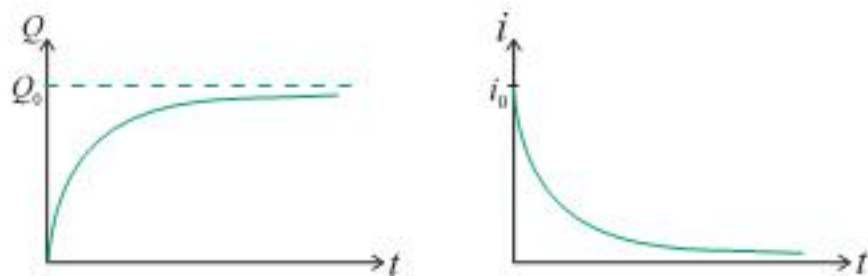
(3) Current:

$$\begin{aligned}
 i &= \frac{dQ}{dt} \\
 &= \mathcal{E}C\left(\frac{1}{RC}\right)e^{-t/RC} \\
 i(t) &= \frac{\mathcal{E}}{R}e^{-t/RC} \\
 \begin{cases} i(t = 0) &= \frac{\mathcal{E}}{R} = \text{Initial current} = i_0 \\ i(t \rightarrow \infty) &= 0 \end{cases}
 \end{aligned}$$




(4) At time = 0, the capacitor acts like *short circuit* when there is *zero charge on the capacitor*.

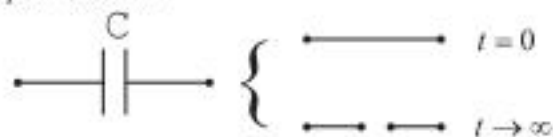(5) As time $\rightarrow \infty$, the capacitor is *fully charged* and current = 0, it acts like a *open circuit*.



- (6) $\tau_c = RC$ is called the **time constant**. It's the time it takes for the charge to reach $(1 - \frac{1}{e}) Q_0 \simeq 0.63Q_0$

(B) *Discharging a charged capacitor:*

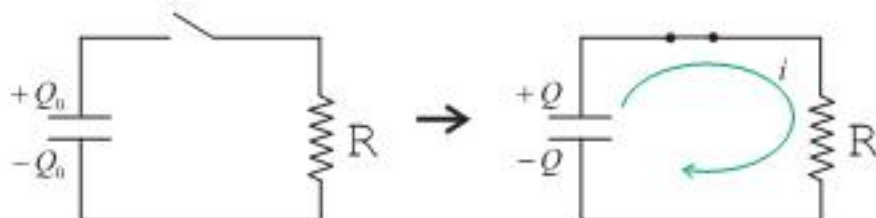

Note: Direction of i is chosen so that the current represents the rate at which the charge on the capacitor is *decreasing*.

$$\therefore i = -\frac{dQ}{dt}$$


Loop Rule:

$$\begin{aligned} V_c - iR &= 0 \\ \Rightarrow \frac{Q}{C} + \frac{dQ}{dt}R &= 0 \\ \Rightarrow \frac{dQ}{dt} &= -\frac{1}{RC}Q \end{aligned}$$

Integrate both sides and use the initial condition:

$$t = 0, \quad Q \text{ on capacitor} = Q_0$$

$$\begin{aligned} \int_{Q_0}^Q \frac{dQ}{Q} &= -\frac{1}{RC} \int_0^t dt \\ \Rightarrow \ln Q - \ln Q_0 &= -\frac{t}{RC} \\ \Rightarrow \ln\left(\frac{Q}{Q_0}\right) &= -\frac{t}{RC} \\ \Rightarrow \frac{Q}{Q_0} &= e^{-t/RC} \\ \Rightarrow Q(t) &= Q_0 e^{-t/RC} \\ (i = -\frac{dQ}{dt}) \Rightarrow i(t) &= \frac{Q_0}{RC} e^{-t/RC} \\ (\text{At } t = 0) \Rightarrow i(t = 0) &= \frac{1}{R} \cdot \underbrace{\frac{Q_0}{C}}_{\text{Initial P.D. across capacitor}} \\ i_0 &= \frac{V_0}{R} \end{aligned}$$

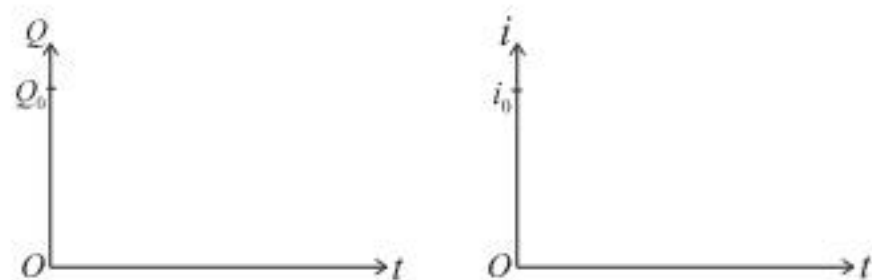

$$\text{At } t = RC = \tau \quad Q(t = RC) = \frac{1}{e} Q_0 \simeq 0.37Q_0$$

Chapter 6


Magnetic Force

6.1 Magnetic Field

For stationary charges, they experienced an **electric force** in an **electric field**.
For moving charges, they experienced a **magnetic force** in a **magnetic field**.

Mathematically, $\vec{F}_E = q\vec{E}$ (electric force)
 $\vec{F}_B = q\vec{v} \times \vec{B}$ (magnetic force)

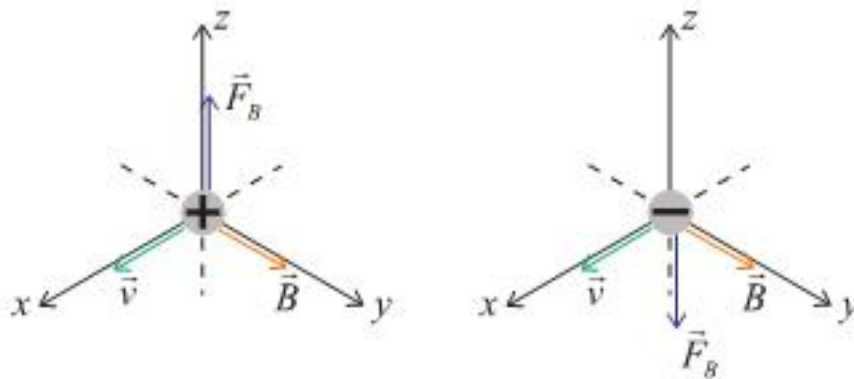Direction of the magnetic force determined from *right hand rule*.



Magnetic field \vec{B} : Unit = Tesla (T)
 $1\text{T} = 1\text{C moving at } 1\text{m/s experiencing } 1\text{N}$

Common Unit: 1 Gauss (G) = $10^{-4}\text{T} \approx$ magnetic field on earth's surface

Example: What's the force on a 0.1C charge moving at velocity $\vec{v} = (10\hat{j} - 20\hat{k})\text{ms}^{-1}$ in a magnetic field $\vec{B} = (-3\hat{i} + 4\hat{k}) \times 10^{-4}\text{T}$

$$\vec{F} = q\vec{v} \times \vec{B}$$

$$\begin{aligned}
 &= +0.1 (10\hat{j} - 20\hat{k}) \times (-3\hat{i} + 4\hat{k}) \times 10^{-4} N \\
 &= 10^{-5} (-30 \cdot -\hat{k} + 40\hat{i} + 60\hat{j} + 0) N
 \end{aligned}$$

Effects of magnetic field is usually quite small.

$$\begin{aligned}
 \vec{F} &= q\vec{v} \times \vec{B} \\
 |\vec{F}| &= qvB \sin\theta, \quad \text{where } \theta \text{ is the angle between } \vec{v} \text{ and } \vec{B}
 \end{aligned}$$

\therefore Magnetic force is *maximum* when $\theta = 90^\circ$ (i.e. $\vec{v} \perp \vec{B}$)

Magnetic force is *minimum* (0) when $\theta = 0^\circ, 180^\circ$ (i.e. $\vec{v} \parallel \vec{B}$)

Graphical representation of B-field: **Magnetic field lines**

Compared with **Electric field lines**:


Similar characteristics :

- (1) Direction of E-field/B-field indicated by *tangent* of the field lines.
- (2) Magnitude of E-field/B-field indicated by *density* of the field lines.

Differences :

- (1) $\vec{F}_E \parallel$ E-field lines; $\vec{F}_B \perp$ B-field lines
- (2) E-field line begins at positive charge and ends at negative charge; B-field line forms a closed loop.

Example : Chap35, Pg803 Halliday

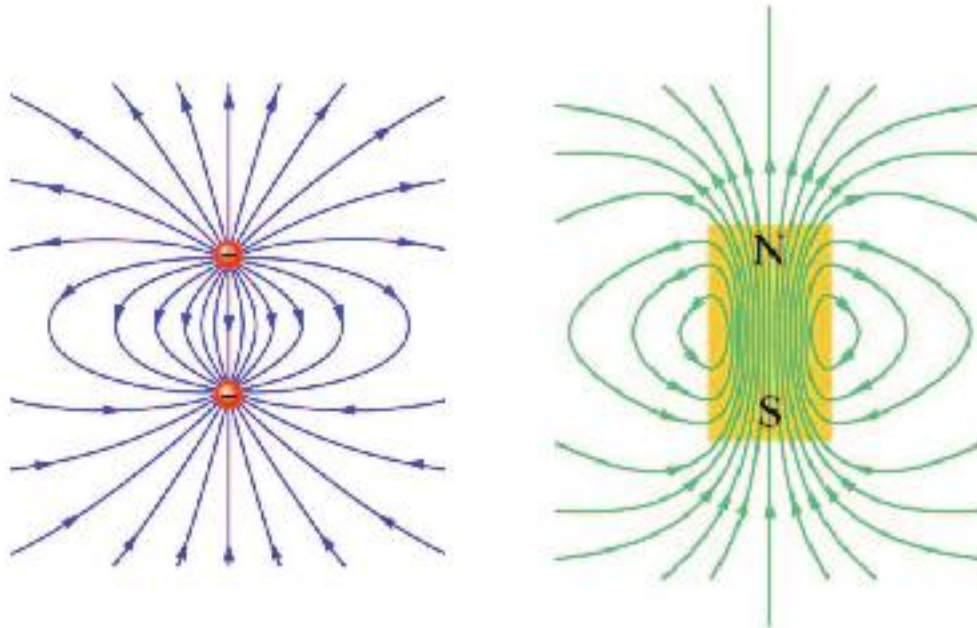


Note: Isolated magnetic monopoles do not exist.

6.2 Motion of A Point Charge in Magnetic Field


Since $\vec{F}_B \perp \vec{v}$, therefore B-field only changes the *direction* of the velocity but not its *magnitude*.

Generally, $\vec{F}_B = q\vec{v} \times \vec{B} = qv_{\perp}B$,

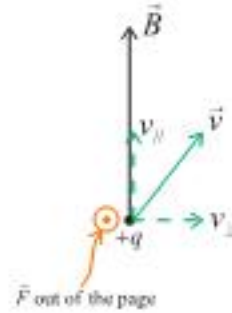\therefore We only need to consider the motion component \perp to B-field.



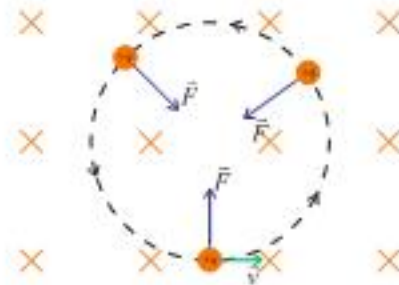We have *circular motion*. Magnetic force provides the *centripetal force* on the moving charge particles.




$$\begin{aligned} \therefore F_B &= m \frac{v^2}{r} \\ |q|vB &= m \frac{v^2}{r} \\ \therefore r &= \frac{mv}{|q|B} \end{aligned}$$

where r is radius of circular motion.

Time for moving around one orbit:

$$T = \frac{2\pi r}{v} = \frac{2\pi m}{qB} \quad \text{Cyclotron Period}$$

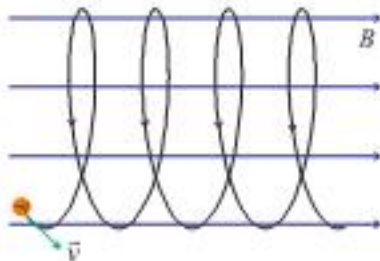- (1) Independent of v (non-relativistic)
- (2) Use it to measure m/q



Generally, charged particles with constant velocity moves in **helix** in the presence of constant B-field.


Note :

- (1) B-field does NO work on particles.
- (2) B-field does NOT change K.E. of particles.

Particle Motion in Presence of E-field & B-field:

$$\boxed{\vec{F} = q\vec{E} + q\vec{v} \times \vec{B}} \quad \text{Lorentz Force}$$

Special Case : $\vec{E} \perp \vec{B}$

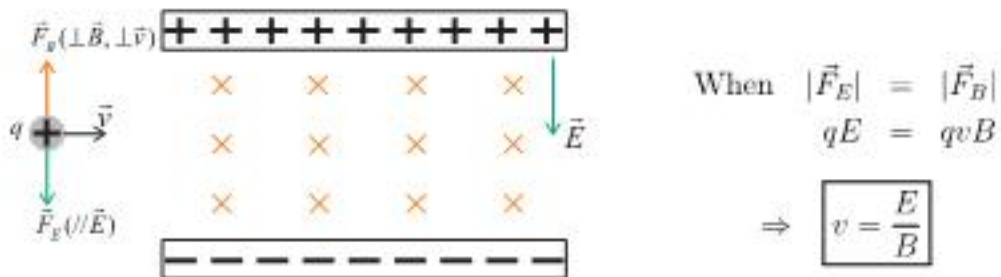

\therefore For charged particles moving at $v = E/B$, they will pass through the crossed E and B fields without vertical displacement.


\Rightarrow **velocity selector**

Applications :


- Cyclotron (Lawrence & Livingston 1934)
- Measuring e/m for electrons (Thomson 1897)
- Mass Spectrometer (Aston 1919)

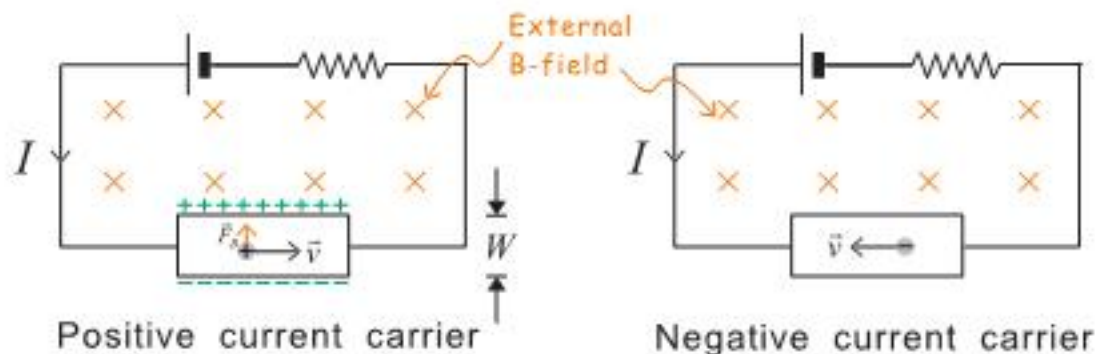6.3 Hall Effect

Charges travelling in a conducting wire will be *pushed to one side of the wire* by the external magnetic field. This separation of charge in the wire is called the **Hall Effect**.



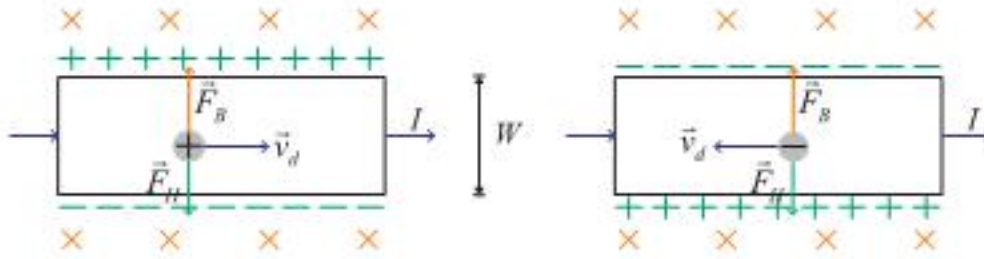The separation will stop when F_B experienced by the current carrier is *balanced* by the force \vec{F}_H caused by the E-field set up by the separated charges.



Define :

$$\begin{aligned} \Delta V_H &= \text{Hall Voltage} \\ &= \text{Potential difference across the conducting strip} \end{aligned}$$

$$\therefore \text{E-field from separated charges: } E_H = \frac{\Delta V_H}{W}$$

where $W = \text{width of conducting strip}$

In equilibrium: $q\vec{E}_H + q\vec{v}_d \times \vec{B} = 0$, where \vec{v}_d is drift velocity

$$\therefore \frac{\Delta V_H}{W} = v_d B$$

Recall from Chapter 5,

$$i = nqAv_d$$

where n is density of charge carrier,

A is cross-sectional area = width \times thickness = $W \cdot t$

$$\therefore \frac{\Delta V_H}{W} = \frac{i}{nqWt} B$$

$$\Rightarrow \boxed{n = \frac{iB}{qt\Delta V_H}} \quad \text{To determine density of charge carriers}$$


Suppose we determine n for a particular metal ($\therefore q = e$), then we can *measure B-field strength by measuring the Hall voltage*:

$$\boxed{B = \frac{net}{i} \Delta V_H}$$

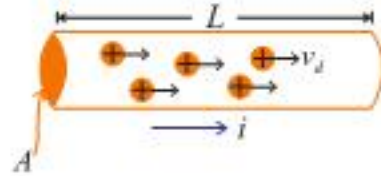6.4 Magnetic Force on Currents

Current = many charges moving together

Consider a wire segment, length L , carrying current i in a magnetic field.



Total magnetic force = $\left(\underbrace{q\vec{v}_d \times \vec{B}}_{\text{force on one charge carrier}} \right) \cdot \underbrace{nAL}_{\text{Total number of charge carrier}}$

Recall $i = nqv_dA$

$$\therefore \boxed{\text{Magnetic force on current } \vec{F} = i\vec{L} \times \vec{B}}$$


where \vec{L} = Vector of which: $|\vec{L}|$ = length of current segment; direction = direction of current

For an infinitesimal wire segment $d\vec{l}$

$$\boxed{d\vec{F} = i d\vec{l} \times \vec{B}}$$

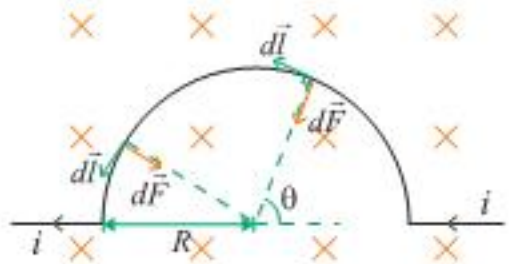Example 1: Force on a semicircle current loop

$$\begin{aligned} d\vec{l} &= \text{Infinitesimal} \\ &\quad \text{arc length element } \perp \vec{B} \\ \therefore dl &= R d\theta \\ \therefore dF &= iRB d\theta \end{aligned}$$



By symmetry argument, we only need to consider vertical forces, $dF \cdot \sin \theta$


$$\begin{aligned} \therefore \text{Net force } F &= \int_0^\pi dF \sin \theta \\ &= iRB \int_0^\pi \sin \theta d\theta \\ F &= 2iRB \quad (\text{downward}) \end{aligned}$$

Method 2: Write $d\vec{l}$ in \hat{i}, \hat{j} components


$$\begin{aligned} d\vec{l} &= -dl \sin \theta \hat{i} + dl \cos \theta \hat{j} \\ &= R d\theta (-\sin \theta \hat{i} + \cos \theta \hat{j}) \\ \vec{B} &= -B \hat{k} \quad (\text{into the page}) \\ \therefore d\vec{F} &= i d\vec{l} \times \vec{B} \\ &= -iRB \sin \theta d\theta \hat{j} - iRB \cos \theta \hat{i} \end{aligned}$$

$$\begin{aligned} \therefore \vec{F} &= \int_0^\pi d\vec{F} \\ &= -iRB \left[\int_0^\pi \sin \theta d\theta \hat{j} + \int_0^\pi \cos \theta d\theta \hat{i} \right] \\ &= -2iRB \hat{j} \end{aligned}$$

Example 2: Current loop in B-field

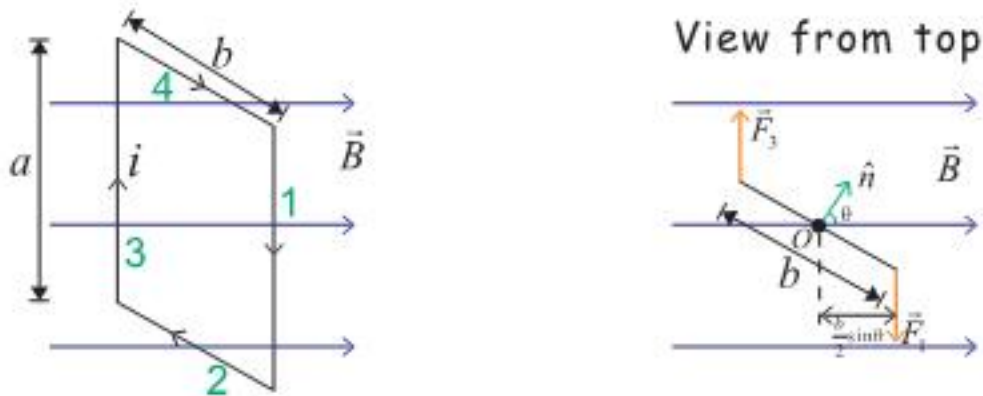


For segment 2:

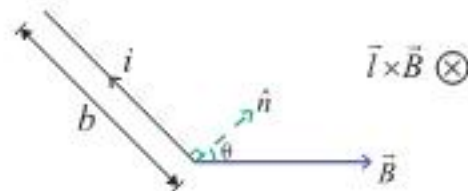

$$F_2 = ibB \sin(90^\circ + \theta) = ibB \cos \theta \quad (\text{pointing downward})$$

For segment 4:

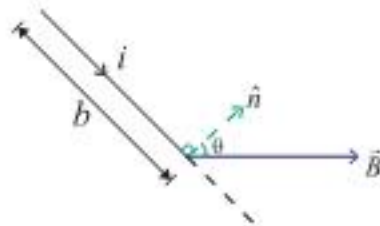

$$F_4 = ibB \sin(90^\circ - \theta) = ibB \cos \theta \quad (\text{pointing upward})$$