

Chapter .2

Algorithms and Design of the Common Fixed-Point Arithmetic Operations




Addition Operation


Addition: is the most frequent operation performed by ALU. It also used for multiplication and division. Thus the speed of the adder unit is essential to the efficient operation of an execution unit.

Half Adder (HA)

 Half adder circuit has two inputs: A and B, which add two input digits and generate a carry and sum.




Inputs		Outputs		Decimal Value
x	y	C	S	
0	0	0	0	0
0	1	0	1	1
1	0	0	1	1
1	1	1	0	2

 


$$S = \bar{x}.y + x.\bar{y} \equiv x \oplus y$$

$$C = x.y$$

Figure: Half-adder

 

 Full Adder (FA): is a combinational digital circuit with I/P bits x_i and y_i and incoming carry bit c_i and O/P sum bit s_i and outgoing carry bit c_{i+1}




x_i	y_i	c_i	c_{i+1}	s_i
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$s_i = x_i y_i' c_i' + x_i' y_i c_i' + x_i' y_i' c_i + x_i y_i c_i \equiv x_i \oplus y_i \oplus c_i$$


$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$



Implementations of FA

 

(b)

 


(c)



Delay of a FA

$$T_{FA} = \max(t_{c_{i+1}}, t_{s_i})$$
 
$$= \max(2t_{NAND}, t_{XOR}) + t_{XOR} = 2t_{XOR}$$



Implementations of FA (continue)

  

Delay of a FA

$$\begin{aligned} T_{FA} &= \max(t_{c_{i+1}}, t_{s_i}) \\ &= \max(2t_{NAND}, t_{XOR}) + t_{XOR} = 2t_{XOR} \end{aligned}$$



Carry Ripple (propagate) Adder (CRA) or CPA

Ripple effect observed at sum outputs of adder until carry propagation is complete.

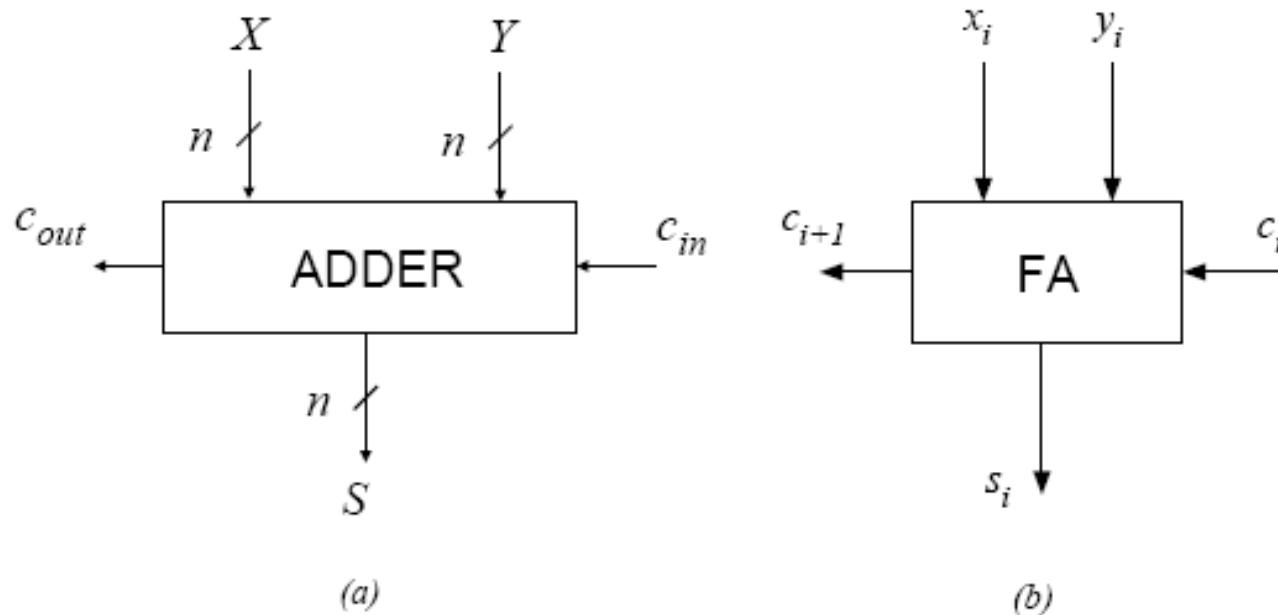


Fig.(2) a: An n- bit adder b: 1- bit adder (FA)



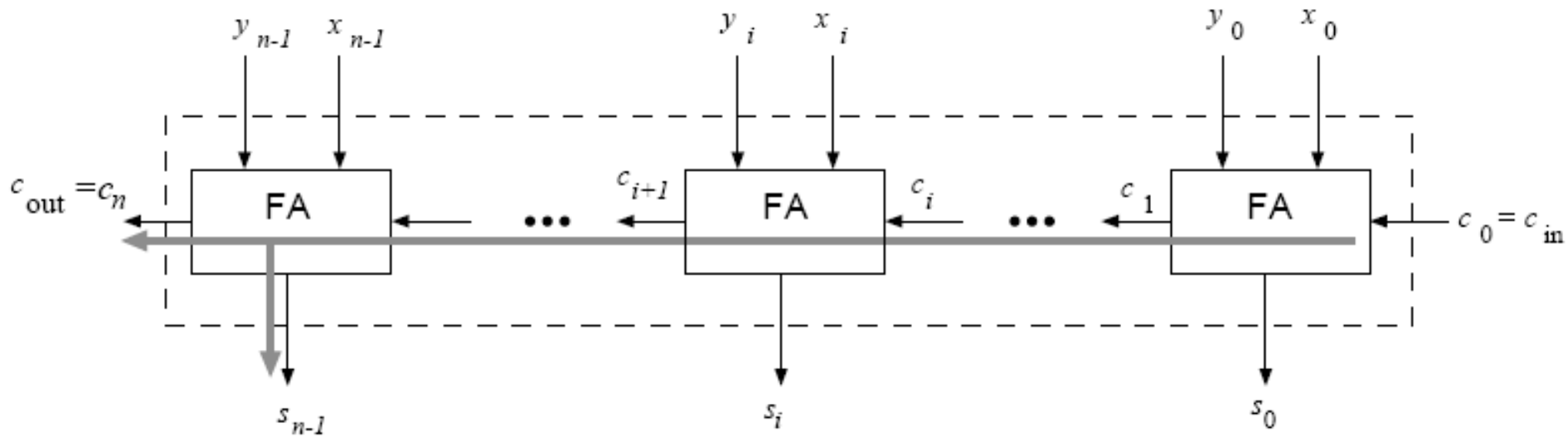


Figure: n-bit carry ripple adder (CRA)

The two (n-bit) operands (X and Y) are available at the same time.

*The carries propagate from the FA in position 0 (with inputs are x_0 and y_0) to position i before that position produces correct sum and carry out bits.

The worst case delay (T_{CRA}) of n-bit CRA

$$T_{CRA} = (n - 1)t_c + \max(t_c, t_s)$$

$$= 2(n - 1)t_{NAND} + \max(2t_{NAND}, t_{XOR}) + t_{XOR}$$

This is the delay of first XOR gate in the sum circuit



Example: Design an 8-bit CRA to add the following 2's complement numbers.
 Perform the addition on your design: $A = -93_{10}$ $B = 126_{10}$

$A = +93_{10} = (01011101)_2$ **Take 1's complement of A:** $A' = (10100010)$

$B = 126_{10} \equiv (01111110)_2$

 


Figure: 8- bit CRA



Reducing the Adder Delay

The delay of the CRA can be reduced by the following approaches:

- Reducing the carry delay t_c . This is achieved in the switched CRA called Manchester adder.
- Changing the linear factor (n) to a smaller factor (such as n/k or \log_n). This is achieved by the carry skip adder, carry lookahead adder, prefix adder, carry select adder, and conditional sum adder.
- Changing the number representation system.



Carry Lookahead Adder (CLA)

The basic idea of CLA is to compute several carries, simultaneously. In the extreme, all carries could be computed at the same time.

Aside: The carry-out from a FA is: $c_{i+1} = x_i y_i + x_i c_i + y_i c_i$

$$c_{i+1} = x_i y_i + (x_i + y_i) c_i$$

From this equation, we can see that there are three **mutually exclusive cases**. These cases depends only on the input operands bits (x_i and y_i).

Case 1: carry c_{i+1} generate if $x_i = y_i = 1 \rightarrow g_i = x_i \cdot y_i$

Case 2: carry c_i is propagated if x_i or $y_i \rightarrow p_i = x_i \oplus y_i$

Case 3: carry c_i is killed if $x_i = y_i = 0 \rightarrow k_i = x_i' \cdot y_i'$

Or is alive if $a_i = k_i'$

*** Rewrite the carry-out of a FA:**

$$c_{i+1} = g_i + a_i c_i \quad \text{or} \quad c_{i+1} = g_i + p_i c_i$$

Return



(n-bit) CLA Addition

Using the previous equations of c_{i+1} \longrightarrow all carries can be determined **in parallel** from the input data **X** and **Y** and forced carry **C₀**.

Example: Design a 4-bit CLA \longrightarrow the carry equations are:

$$c_1 = g_0 + c_0 a_0$$

$$c_2 = g_1 + c_1 a_1 = g_1 + g_0 a_1 + c_0 a_0 a_1$$

$$c_3 = g_2 + c_2 a_2 = g_2 + g_1 a_2 + g_0 a_1 a_2 + c_0 a_0 a_1 a_2$$

$$c_4 = g_3 + c_3 a_3 = g_3 + g_2 a_3 + g_1 a_2 a_3 + g_0 a_1 a_2 a_3 + c_0 a_0 a_1 a_2 a_3$$

The internal design of a 4-bit CLA is:



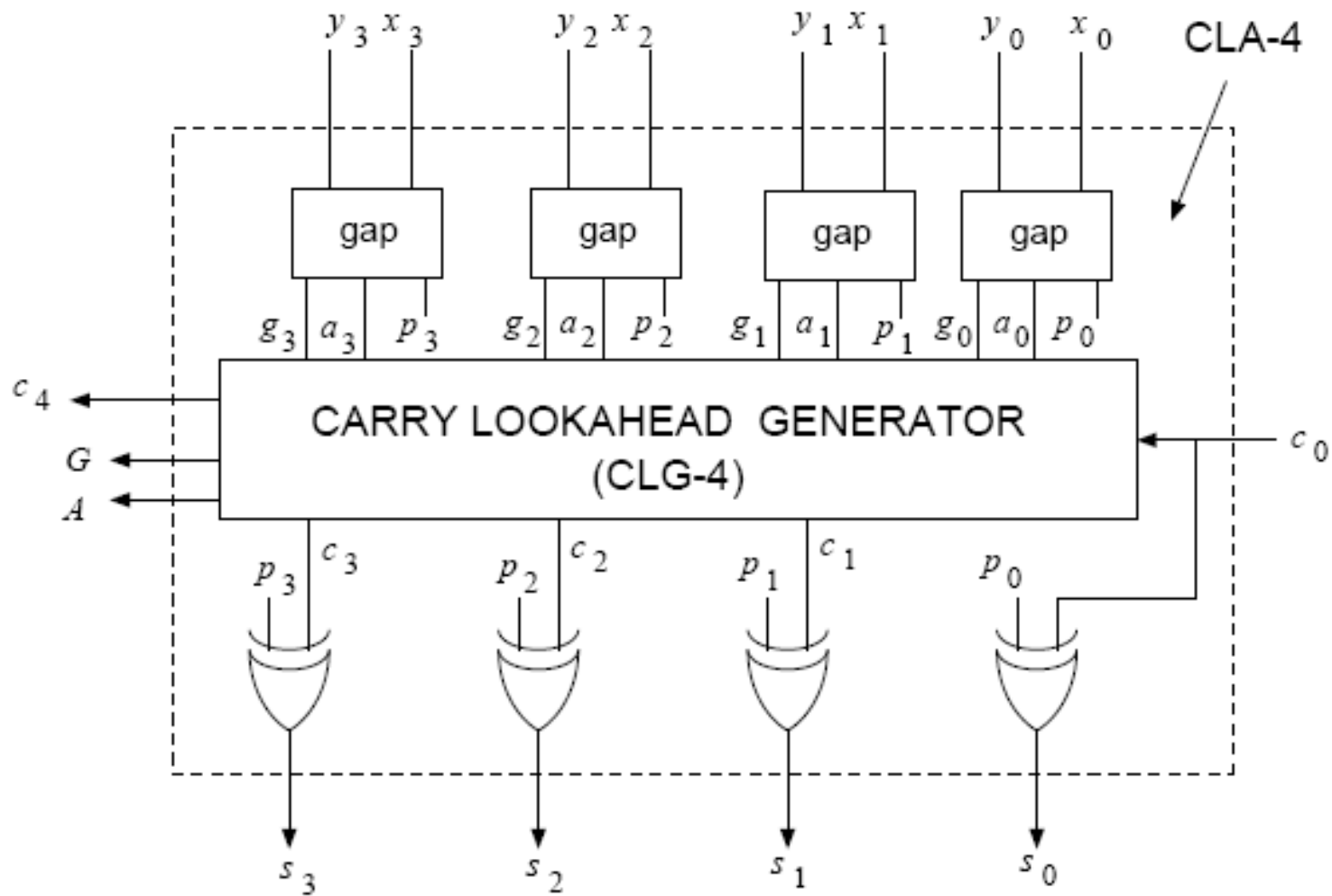


Fig. (4)- bit CLA module ($m=4$)

Ex. Add $X = 8_{10} = (1000)_2$, and $Y = 9_{10} = (1001)_2$



 
 


Figure: Internal logic design of gap circuit.

Where

A: is a carry alive signal of the group "m" (where m= 4-bit) :

$$A = \underset{i=0}{\text{AND}}^{m-1} a_i$$

and G: is a carry generate signal of the group m ($m= 4$ -bit) :

$$G = \underset{j=0}{\text{OR}}^{m-1} \left(\underset{i=j+1}{\text{AND}}^{m-1} a_i \right) g_j$$

