

# CHAPTER 11

---

## LATCHES AND FLIP-FLOPS

# Contents

---

- 11.1 Introduction
- 11.2 Set-Reset Latch
- 11.3 Gated D Latch
- 11.4 Edge-Triggered D Flip-Flop
- 11.5 S-R Flip-Flop
- 11.6 J-K Flip-Flop
- 11.7 T Flip-Flop
- 11.8 Flip-Flop with Additional Inputs
- 11.9 Summary

# Objectives


---

1. Explain in words the operation of S-R and gated D latches
2. Explain in words the operation of D, D-CE, S-R, J-K and T flip-flops
3. Make a table and derive the characteristic (next-state) equation for such latches and flip-flops. State any necessary restrictions on the input signals
4. Draw a timing diagram relating the input and output of such latches flip-flops
5. Show how latches and flip-flops can be constructed using gates. Analyze the operation of a flip-flop that is constructed of gates and latches

# 11.1 Introduction

To construct a switching circuit has a memory, must introduce *feedback* to circuit

Fig 11-1.

 

(a) Inverter with feedback




→ Unstable state


(b) Oscillation at inverter output

Fig 11-2.

→ Stable state

 

(a)

 

(b)

# 11.2 Set-Reset Latch

Fig 11-3.  $S=R=0 (Q=0) \rightarrow S=1, R=0$


 
 
 


Fig 11-4.  $S=R=0 (Q=1) \rightarrow S=0, R=1$

 

# 11.2 Set-Reset Latch

Fig 11-5. S-R Latch(cross-coupled structure)


 


Fig 11-6. Improper S-R Latch Operation ( $S=R=1$ ; prohibited)

 

# 11.2 Set-Reset Latch

Fig 11-7. Timing Diagram for S-R Latch

 


Table 11-1. S-R Latch Operation

$S(t)$	$R(t)$	$Q(t)$	$Q(t+\epsilon)$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	-
1	1	1	-

} Inputs not allowed

# 11.2 Set-Reset Latch

Fig 11-8. Map for  $Q(t+\epsilon)$


 



Fig 11-9. Switch Debouncing with an S-R Latch

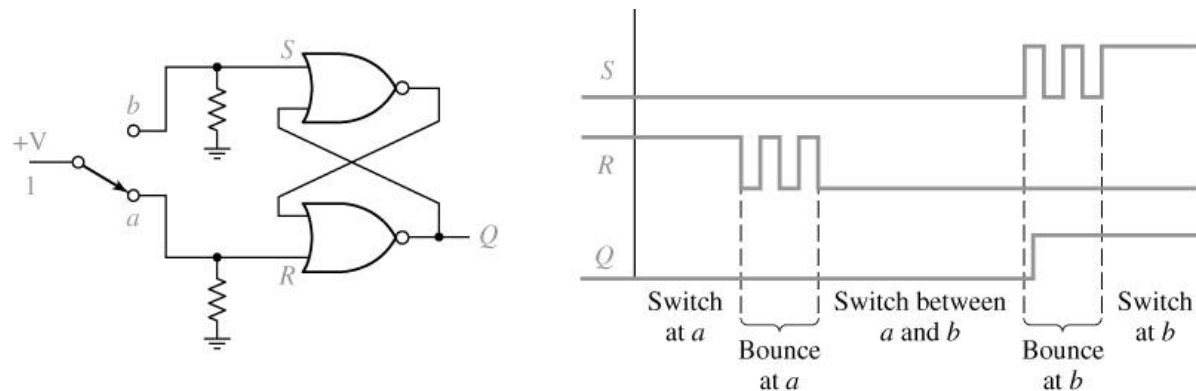




# 11.2 Set-Reset Latch

Fig 11-10.  $\bar{S} - \bar{R}$  Latch

 

(a)

 

(b)

$S$	$R$	$Q$	$Q^+$
1	1	0	0
1	1	1	1
1	0	0	0
1	0	1	0
0	1	0	1
0	1	1	1
0	0	0	-
0	0	1	-

} Inputs not allowed

(c)

# 11.3 Gated D Latch

Figure 11-11. Gated D Latch

 


Figure 11-12. Symbol and Truth Table for Gated Latch


	$G$	$D$	$Q$	$Q^+$
	0	0	0	0
	0	0	1	1
	0	1	0	0
	0	1	1	1
	1	0	0	0
	1	0	1	0
	1	1	0	1
	1	1	1	1

$GD$		00	01	11	10
$Q$	0	0	0	1	0
	1	1	1	1	0


$Q^+ = G'Q + GD$

# 11.4 Edge-Triggered D Flip-Flop

Figure 11-13. D Flip-Flops

 

(a) Rising-edge trigger

 


(b) Falling-edge trigger

$D$	$Q$	$Q^+$
0	0	0
0	1	0
1	0	1
1	1	1

(c) Truth table

$$Q^+ = D$$

Figure 11-14. Timing for D Flip-Flop (Falling-Edge Trigger)

 

# 11.4 Edge-Triggered D Flip-Flop

Figure 11-15. D Flip-Flop (Rising-Edge Trigger)



 


Figure 11-16. Setup and Hold Times for an Edge-Triggered D Flip-Flop

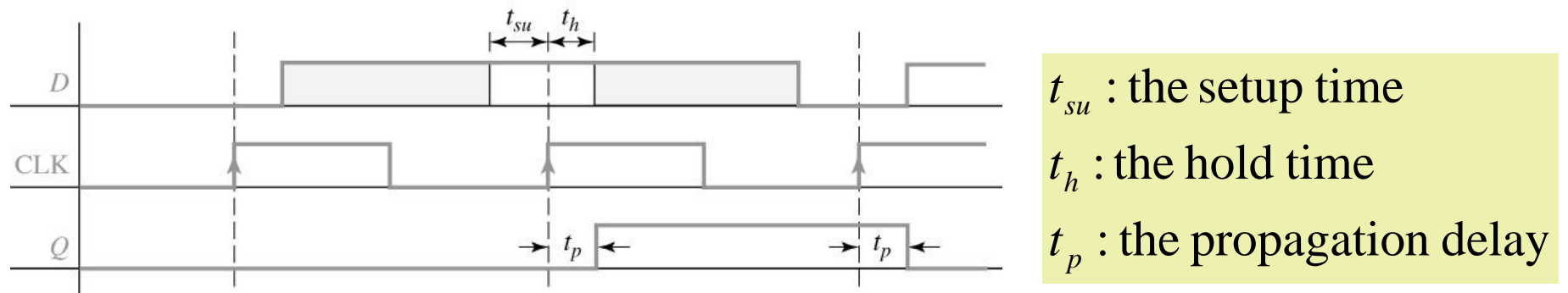


# 11.4 Edge-Triggered D Flip-Flop


Figure 11–17. Determination of Minimum Clock Period

 


(a) Simple flip-flop circuit

 

(b) Setup time not satisfied

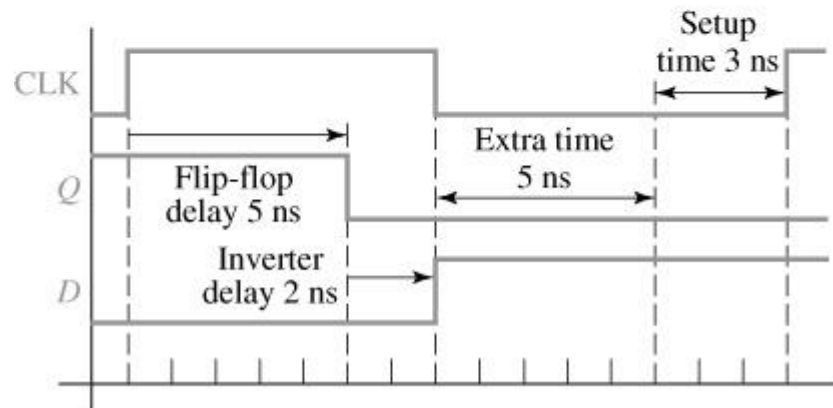


(c) Setup time satisfied

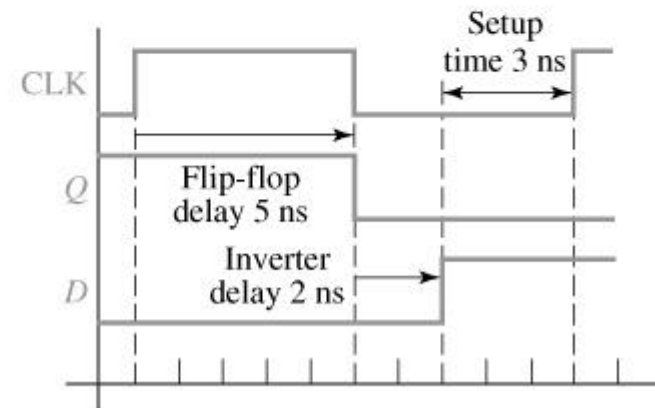

(d) Minimum clock period

# 11.5 S-R Flip-Flop


Figure 11-18. S-R Flip-Flop

 


Operation summary :

$S=R=0$	No state change
$S=1, R=0$	Set $Q$ to 1 (after active Ck edge)
$S=0, R=1$	Reset $Q$ to 0 (after active Ck edge)
$S=R=1$	Not allowed

Figure 11-19. S-R Flip-Flop Implementation and Timing

 


(a) Implementation with two latches

 

(b) Timing analysis

# 11.6 J-K Flip-Flop

Figure 11-20. J-K Flip-Flop (Q Changes on the Rising Edge)

 


(a) J-K flip-flop

$J$	$K$	$Q$	$Q^+$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

(b) Truth table and characteristic equation


$$Q^+ = JQ' + K'Q$$

 

(c) J-K flip-flop timing

# 11.6 J-K Flip-Flop


Figure 11-21. Master-Slave J-K Flip-Flop (Q Changes on Rising Edge)

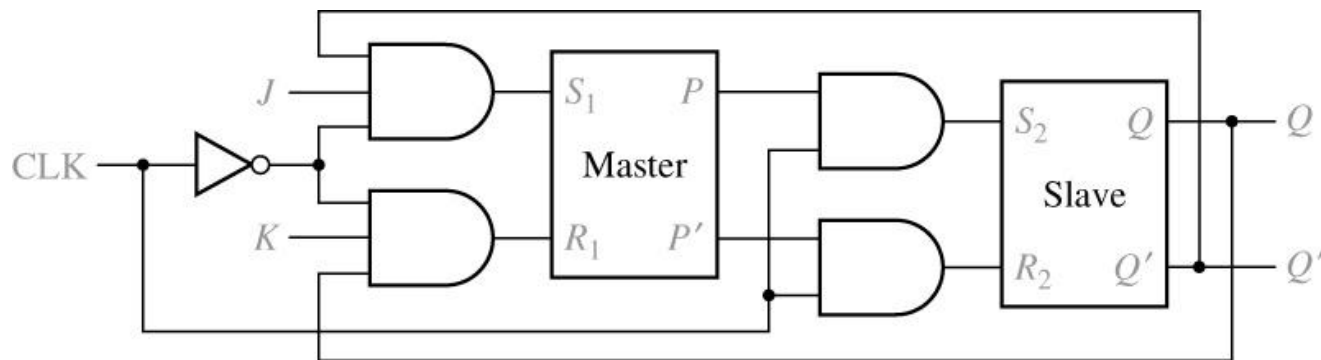



# 11.7 T Flip-Flop

Figure 11-22. T Flip-Flop

 


$$Q^+ = T'Q + TQ' = T \oplus Q$$

(a)


(b)

Figure 11-23. Timing Diagram for T Flip-Flop (Falling-Edge Trigger)

 

# 11.7 T Flip-Flop

Figure 11-24. Implementation of T Flip-Flop

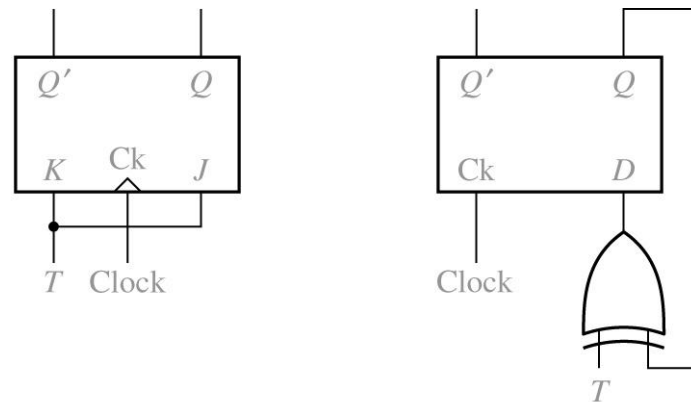

(a) Conversion of J-K to  $T$

(b) Conversion of  $D$  to  $T$

$$Q^+ = JQ' + K'Q = TQ' + T'Q$$

# 11.8 Flip-Flops with Additional Inputs

Figure 11–25. D Flip-Flop with Clear and Preset



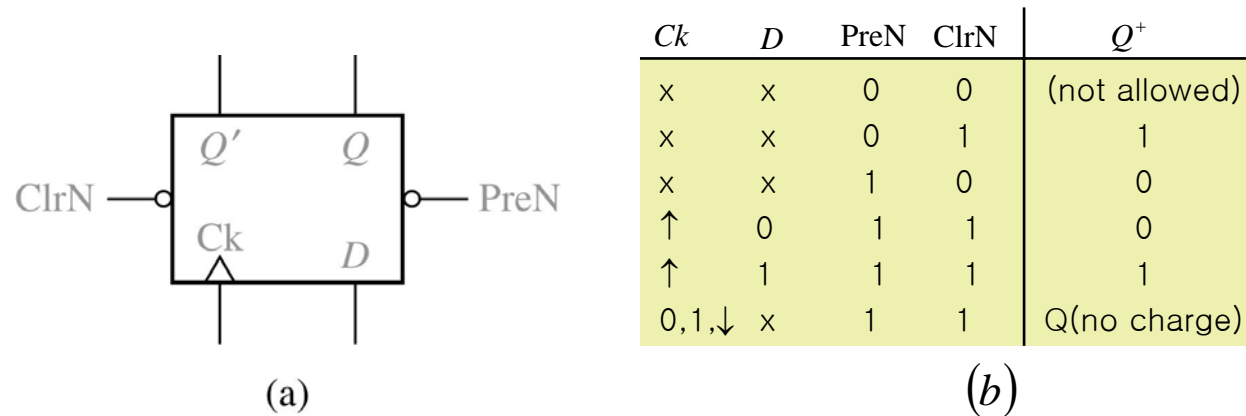


Figure 11–26. Timing Diagram for D Flip-Flop with Asynchronous Clear and Preset

 

# 11.8 Flip-Flops with Additional Inputs

Figure 11-27. D Flip-Flop with Clock Enable

 

The characteristic equation :  $Q^+ = Q \cdot CE' + D \cdot CE$

The MUX output :  $Q^+ = D = Q \cdot CE' + D_{in} \cdot CE$

## 11.9 Summary

---

$$Q^+ = S + R'Q \quad (SR = 0)$$

(S-R latch or flip-flop)

$$Q^+ = GD + G'Q$$

(gated D latch)

$$Q^+ = D$$

(D flip-flop)

$$Q^+ = D \cdot CE + Q \cdot CE'$$

(D-CE flip-flop)

$$Q^+ = JQ' + K'Q$$

(J-K flip-flop)

$$Q^+ = T \oplus Q = T'Q + TQ'$$

(T flip-flop)